

# Σχεδίαση Ψηφιακών Συστημάτων - Εργασία Θεωρίας (Μέρος 5)

Χρήστος Μαργιώλης

Ιούλιος 2020

# Περιεχόμενα

<b>1</b>	<b>Κώδικας και τεκμηρίωση</b>	<b>1</b>
1.1	instrmem.vhd . . . . .	1
1.2	instrmem_tb.vhd . . . . .	2
1.3	datamem.vhd . . . . .	3
1.4	datamem_tb.vhd . . . . .	4
<b>2</b>	<b>Εκτέλεση</b>	<b>7</b>
2.1	instrmem_tb . . . . .	7
2.2	datamem_tb . . . . .	7

## 1 Κώδικας και τεκμηρίωση

### 1.1 instrmem.vhd

Το παρακάτω κύκλωμα υλοποιεί την μνήμη εντολών του MIPS. Ο κώδικας είναι ίδιος με αυτόν της εκφώνησης, απλώς με λίγο διαφορετική μορφοποίηση. Επίσης, στην θέση μνήμης 6 έχει τοποθετηθεί και η εντολή add \$4 \$5 \$6.

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;
use ieee.numeric_std.all;

entity instrmem is port (
    addr:    in std_logic_vector(31 downto 0);
    c:       out std_logic_vector(31 downto 0)
);
end instrmem;

architecture dataflow of instrmem is

type instr_arr is array(0 to 15) of std_logic_vector (31 downto 0);
constant instr_mem: instr_arr := (
    "11111111111111111111111111111111", -- 0
    "1000101010010101010101000011101111", -- 1
    "11111111111111111111111111111111", -- 2
    "00000000000000000000000000000000", -- 3
    "11111111111111111111111111111111", -- 4
    "00000000000000000000000000000000", -- 5
    "0000000001010011000100000001000000", -- 6
    "11111111111111111111111111111111", -- 7
    "11111111111111111111111111111111", -- 8
    "11111111111111111111111111111111", -- 9
    "10101010101011110000101110001010", -- 10
    "11111111111111110000000000000000", -- 11
```

```

        "10001011101010111010111101010111", -- 12
        "11111111111111111111111111111111", -- 13
        "10110111000111010101010101111111", -- 14
        "11111111111111111111111111111111" -- 15
    );

begin
    c <= instr_mem(to_integer(unsigned(addr)));
end dataflow;

```

## 1.2 instrmem\_tb.vhd

Testbench για την μνήμη εντολών του MIPS. Δίνουμε διάφορες τιμές θέσεων μνήμης και η έξοδος είναι τα περιεχόμενα της μνήμης στις θέσεις αυτές.

```
library ieee;
use ieee.std_logic_1164.all;

entity instrmem_tb is
end instrmem_tb;

architecture behav of instrmem_tb is

    signal s_addr: std_logic_vector(3 downto 0);
    signal s_c:    std_logic_vector(31 downto 0);

    component instrmem is port (
        addr: in std_logic_vector(3 downto 0);
        c:    out std_logic_vector(31 downto 0)
    );
end component;

begin

    uut: instrmem port map (
        addr => s_addr,
        c => s_c
    );

    process begin
        s_addr <= "0001";
        wait for 250 ns;

        s_addr <= "0010";
        wait for 250 ns;

        s_addr <= "0110";
        wait for 250 ns;

        s_addr <= "1000";
        wait for 250 ns;

        s_addr <= "1010";
        wait for 250 ns;
    end process;
end behav;
```

### 1.3 datamem.vhd

Το παρακάτω κύκλωμα υλοποιεί την μνήμη εντολών του MIPS. Ο κώδικας είναι ίδιος με αυτόν της εκφώνησης, απλώς με λίγο διαφορετική μορφοποίηση.

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;
use ieee.numeric_std.all;

entity datamem is port (
    clk:    in std_logic;
    addr:   in std_logic_vector(5 downto 0);
    we:     in std_logic;
    re:     in std_logic;
    writed: in std_logic_vector(31 downto 0);
    readd:  out std_logic_vector(31 downto 0)
);
end datamem;

architecture behav of datamem is

    type data_arr is array(0 to 63) of std_logic_vector(31 downto 0);
    signal memfile: data_arr;

begin
    process (clk) begin
        if (clk'event and clk = '0') then
            if we = '1' then
                memfile(to_integer(unsigned(addr))) <= writed;
            end if;
        end if;
        if re = '1' then
            readd <= memfile(to_integer(unsigned(addr)));
        end if;
    end process;
end behav;
```

## 1.4 datamem\_tb.vhd

Testbench για την μνήμη εντολών του MIPS. Οι τιμές για το testbench πάρθηκαν από την εκφώνηση της άσκησης.

```
library ieee;
use ieee.std_logic_1164.all;

entity datamem_tb is
end datamem_tb;

architecture behav of datamem_tb is

    signal s_clk:          std_logic;
    signal s_addr:         std_logic_vector(5 downto 0);
    signal s_we:           std_logic;
    signal s_re:           std_logic;
    signal s_writed:        std_logic_vector(31 downto 0);
    signal s_readd:         std_logic_vector(31 downto 0);

    component datamem is port (
        clk:                in std_logic;
        addr:               in std_logic_vector(5 downto 0);
        we:                 in std_logic;
        re:                 in std_logic;
        writed:              in std_logic_vector(31 downto 0);
        readd:               out std_logic_vector(31 downto 0)
    );
end component;

begin

    uut: datamem port map (
        clk => s_clk,
        addr => s_addr,
        we => s_we,
        re => s_re,
        writed => s_writed,
        readd => s_readd
    );

    process begin
        s_clk <= '0';
        wait for 250 ns;

        s_clk <= '1';
        wait for 250 ns;
```

```

s_we <= '1';
s_re <= '0';
s_addr <= "000000";
s_writed <= "010101010101010101010101010101";
wait for 250 ns;

s_clk <= '0';
wait for 250 ns;

s_clk <= '1';
wait for 250 ns;

s_addr <= "000001";
s_writed <= "11011101110111011101110111011101";
wait for 250 ns;

s_clk <= '0';
wait for 250 ns;

s_clk <= '1';
wait for 250 ns;

s_addr <= "000010";
s_writed <= "00100010001000100010001000100010";
wait for 250 ns;

s_clk <= '0';
wait for 250 ns;

s_clk <= '1';
wait for 250 ns;

s_addr <= "000011";
s_writed <= "10011001100110011001100110011001";
wait for 250 ns;

s_clk <= '0';
wait for 250 ns;

s_clk <= '1';
wait for 250 ns;

s_we <= '0';
s_re <= '1';
s_addr <= "000000";
wait for 250 ns;


```

```
s_clk <= '0';  
wait for 250 ns;  
  
s_clk <= '1';  
wait for 250 ns;  
  
s_addr <= "000001";  
wait for 250 ns;  
  
s_clk <= '0';  
wait for 250 ns;  
  
s_clk <= '1';  
wait for 250 ns;  
end process;  
end behav;
```



## 2 Εκτέλεση

### 2.1 instrmem\_tb

 

### 2.2 datamem\_tb

