

Σχεδίαση Ψηφιακών Συστημάτων - Εργασία Θεωρίας (Μέρος 4)

Χρήστος Μαργιώλης

Ιούλιος 2020

Περιεχόμενα

1	Κώδικας και τεκμηρίωση	1
1.1	ctrl.vhd	1
1.2	ctrl_tb.vhd	2
1.3	sign_ext.vhd	4
1.4	sign_ext_tb.vhd	5
1.5	shl2.vhd	6
1.6	shl2_tb.vhd	7
2	Εκτέλεση	8
2.1	ctrl_tb	8
2.2	sign_ext_tb	8
2.3	shl2_tb	8

1 Κώδικας και τεκμηρίωση

1.1 ctrl.vhd

Το παρακάτω κύκλωμα υλοποιεί την μονάδα ελέγχου ενός επεξεργαστή. Η υλοποίηση έγινε με βάση τον πίνακα από τις διαφάνειες του μαθήματος. Στο τέλος προτίμησα την δομή with-select για πιο ευανάγνωστο κώδικα.

```
library ieee;
use ieee.std_logic_1164.all;
```

```
entity ctrl is port (
    funct:      in std_logic_vector(5 downto 0);
    reg_dst:    out std_logic;
    reg_wr:     out std_logic;
    alu_src:    out std_logic;
    branch:     out std_logic;
    mem_rd:     out std_logic;
    mem_wr:     out std_logic;
    mem_toreg:  out std_logic;
    alu_op:     out std_logic_vector(1 downto 0)
);
end ctrl;
```

```
architecture dataflow of ctrl is
begin
```

```
    reg_dst    <= '1' when funct = "000000" else '0';
    reg_wr     <= '1' when funct = "000000" or funct = "100011" else '0';
    alu_src    <= '1' when funct = "100011" or funct = "101011" else '0';
    branch     <= '1' when funct = "000100" else '0';
    mem_rd     <= '1' when funct = "100011" else '0';
    mem_wr     <= '1' when funct = "101011" else '0';
```

```
mem_toreg      <= '1' when funct = "100011" else '0';
with funct select
    alu_op <= "10" when "000000",
              "01" when "000100",
              "00" when others;
end dataflow;
```

1.2 ctrl_tb.vhd

Testbench για την μονάδα ελέγχου.

```
library ieee;
use ieee.std_logic_1164.all;

entity ctrl_tb is
end ctrl_tb;

architecture behav of ctrl_tb is

    signal s_funct:          std_logic_vector(5 downto 0);
    signal s_reg_dst:        std_logic;
    signal s_reg_wr:         std_logic;
    signal s_alu_src:        std_logic;
    signal s_branch:         std_logic;
    signal s_mem_rd:         std_logic;
    signal s_mem_wr:         std_logic;
    signal s_mem_toreg:      std_logic;
    signal s_alu_op:         std_logic_vector(1 downto 0);

    component ctrl is port (
        funct:          in std_logic_vector(5 downto 0);
        reg_dst:        out std_logic;
        reg_wr:         out std_logic;
        alu_src:        out std_logic;
        branch:         out std_logic;
        mem_rd:         out std_logic;
        mem_wr:         out std_logic;
        mem_toreg:      out std_logic;
        alu_op:         out std_logic_vector(1 downto 0)
    );
end component;

begin

    uut: ctrl port map (
        funct => s_funct,
        reg_dst => s_reg_dst,
        reg_wr => s_reg_wr,
        alu_src => s_alu_src,
        branch => s_branch,
        mem_rd => s_mem_rd,
        mem_wr => s_mem_wr,
        mem_toreg => s_mem_toreg,
        alu_op => s_alu_op
    );
```

```
);  
  
process begin  
    s_funct <= "000000";  
    wait for 250 ns;  
  
    s_funct <= "100011";  
    wait for 250 ns;  
  
    s_funct <= "101011";  
    wait for 250 ns;  
  
    s_funct <= "000100";  
    wait for 250 ns;  
end process;  
end behav;
```

1.3 sign_ext.vhd

Το παρακάτω κύκλωμα υλοποιεί την μονάδα επέκτασης προσήμου. Στην αρχιτεκτονική της, ορίζουμε την έξοδο σε (XXXX συμβολίζει την είσοδο instruction):

- 0x0000XXXX όταν το MSB του instruction είναι 0.
- 0xffffXXXX όταν το MSB είναι 1.

```
library ieee;
use ieee.std_logic_1164.all;

entity sign_ext is port (
    instr:      in std_logic_vector(15 downto 0);
    sign_ex:    out std_logic_vector(31 downto 0)
);
end sign_ext;

architecture dataflow of sign_ext is
begin
    -- Check the MSB to determine the sign.
    sign_ex <= x"0000" & instr when instr(15) = '0' else
               x"ffff" & instr when instr(15) = '1';
end dataflow;
```

1.4 sign_ext_tb.vhd

Testbench για την μονάδα επέκτασης προσήμου.

```
library ieee;
use ieee.std_logic_1164.all;

entity sign_ext_tb is
end sign_ext_tb;

architecture behav of sign_ext_tb is

    signal s_instr:          std_logic_vector(15 downto 0);
    signal s_sign_ex:        std_logic_vector(31 downto 0);

    component sign_ext is port (
        instr:               in std_logic_vector(15 downto 0);
        sign_ex:             out std_logic_vector(31 downto 0)
    );
end component;

begin

    uut: sign_ext port map (
        instr => s_instr,
        sign_ex => s_sign_ex
    );

    process begin
        s_instr <= x"0010";
        wait for 250 ns;

        s_instr <= x"1001";
        wait for 250 ns;

        s_instr <= x"80a0";
        wait for 250 ns;
    end process;
end behav;
```

1.5 shl2.vhd

Το παρακάτω κύκλωμα υλοποιεί μία μονάδα αριστερής ολίσθησης κατά 2 bit. Η αρχιτεκτονική της είναι πολύ απλή: παίρνουμε τα 30 τελευταία bit της εισόδου και τους «κολλάμε» (concatenate) 2 μηδενικά bit στο τέλος.

```
library ieee;
use ieee.std_logic_1164.all;

entity shl2 is port (
    in1:    in std_logic_vector(31 downto 0);
    d:      out std_logic_vector(31 downto 0)
);
end shl2;

architecture dataflow of shl2 is
begin
    d <= in1(29 downto 0) & "00";
end dataflow;
```


1.6 shl2_tb.vhd

Testbench για την μονάδα αριστερής ολίσθησης κατά 2 bit.

```
library ieee;
use ieee.std_logic_1164.all;

entity shl2_tb is
end shl2_tb;

architecture behav of shl2_tb is

    signal s_in1:    std_logic_vector(31 downto 0);
    signal s_d:      std_logic_vector(31 downto 0);

    component shl2 is port (
        in1:    in std_logic_vector(31 downto 0);
        d:      out std_logic_vector(31 downto 0)
    );
end component;

begin


    uut: shl2 port map (
        in1 => s_in1,
        d => s_d
    );

    process begin
        s_in1 <= x"0000aaaf";
        wait for 250 ns;


        s_in1 <= x"ffffaaaf";
        wait for 250 ns;
    end process;
end behav;
```

2 Εκτέλεση

2.1 ctrl_tb

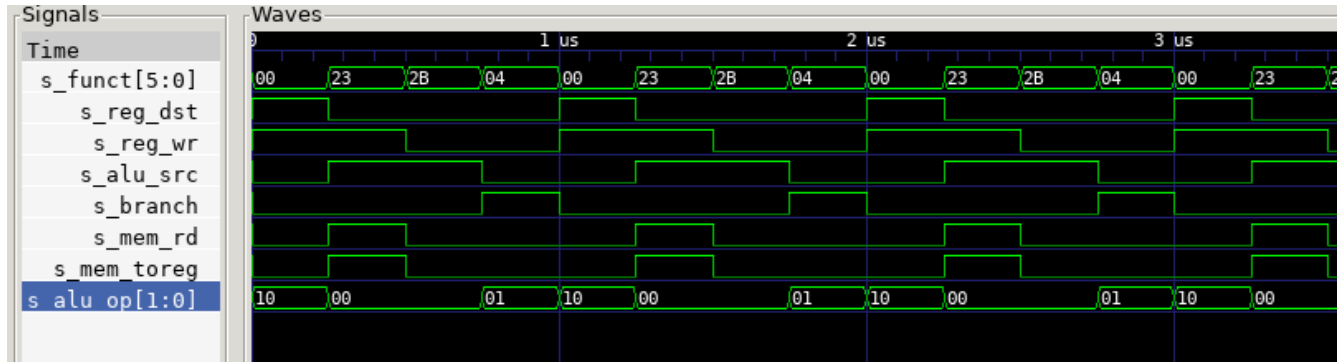

2.2 sign_ext_tb

 

2.3 shl2_tb

