

Σχεδίαση Ψηφιακών Συστημάτων - Εργασία Θεωρίας (Μέρος 6)

Χρήστος Μαργιώλης

Ιούλιος 2020

Περιεχόμενα

1	Κώδικας και τεκμηρίωση	1
1.1	reg.vhd	1
1.2	reg_tb.vhd	2
1.3	regfile.vhd	4
1.4	regfile_tb.vhd	5
1.5	regfile_ext.vhd	7
1.6	regfile_ext_tb.vhd	9
2	Εκτέλεση	12
2.1	reg_tb	12
2.2	regfile_tb	12
2.3	regfile_ext_tb	12

1 Κώδικας και τεκμηρίωση

1.1 reg.vhd

Το παρακάτω κύκλωμα υλοποιεί έναν καταχωρητή. Ο κώδικας είναι παραμετροποιημένος για να μπορεί να μετατραπεί στο επόμενο μέρος σε 32-bit χωρίς αλλαγές.

```
library ieee;
use ieee.std_logic_1164.all;

entity reg is
generic (
    sz:      natural := 4
);
port (
    d:       in std_logic_vector(sz-1 downto 0);
    rst:     in std_logic;
    clk:     in std_logic;
    q:       out std_logic_vector(sz-1 downto 0)
);
end reg;

architecture behav of reg is

    -- We want to automatically initialize the vector no matter its size.
    signal s_init: std_logic_vector(sz-1 downto 0) := (others => '0');

begin
    process (rst, clk) begin
        if (rst = '0') then
            q <= s_init;
        end if;
    end process;
end behav;
```

```
        elsif (rising_edge(clk)) then
            q <= d;
        end if;
    end process;
end behav;
```

1.2 reg_tb.vhd

Testbench για τον καταχωρητή.

```
library ieee;
use ieee.std_logic_1164.all;

entity reg_tb is
end reg_tb;

architecture behav of reg_tb is

    signal s_sz:    natural := 4;
    signal s_d:     std_logic_vector(s_sz-1 downto 0);
    signal s_rst:   std_logic;
    signal s_clk:   std_logic;
    signal s_q:     std_logic_vector(s_sz-1 downto 0);

    component reg is
    generic (
        sz:    natural := 4
    );
    port (
        d:      in std_logic_vector(s_sz-1 downto 0);
        rst:    in std_logic;
        clk:    in std_logic;
        q:      out std_logic_vector(s_sz-1 downto 0)
    );
end component;

begin

    uut: reg port map (
        d => s_d,
        rst => s_rst,
        clk => s_clk,
        q => s_q
    );

    process begin
        s_rst <= '1';
        s_clk <= '0';
        s_d <= "0010";
        wait for 250 ns;

        s_clk <= '1';
        wait for 250 ns;
```

```
s_clk <= '0';
s_d <= "1110";
wait for 250 ns;

s_clk <= '1';
wait for 250 ns;

s_clk <= '0';
s_d <= "1010";
wait for 250 ns;

s_rst <= '0';
s_clk <= '1';
wait for 250 ns;
end process;
end behav;
```

1.3 regfile.vhd

Το παρακάτω κύκλωμα υλοποιεί ένα register file.

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;
use ieee.numeric_std.all;

entity regfile is
generic (
    sz:      natural := 4;
    addrw:   natural := 3
);
port (
    idata:   in std_logic_vector(sz-1 downto 0);
    addr:    in std_logic_vector(addrw-1 downto 0);
    we:      in std_logic;
    clk:     in std_logic;
    odata:   out std_logic_vector(sz-1 downto 0)
);
end regfile;

architecture behav of regfile is

    signal arrsz:   natural := 4;
    type regarr     is array(arrsz-1 downto 0) of std_logic_vector(sz-1 downto 0);
    signal regf:    regarr;

begin
    process (clk) begin
        if (clk'event and clk = '0') then
            if (we = '1') then
                regf(to_integer(unsigned(addr))) <= idata;
            end if;
        end if;
    end process;
    odata <= regf(to_integer(unsigned(addr)));
end behav;
```

1.4 regfile_tb.vhd

Testbench για το register file.

```
library ieee;
use ieee.std_logic_1164.all;

entity regfile_tb is
end regfile_tb;

architecture behav of regfile_tb is

  component regfile is
    generic (
      sz:      natural := 4;
      addrw:   natural := 3
    );
    port (
      idata:   in std_logic_vector(sz-1 downto 0);
      addr:    in std_logic_vector(addrw-1 downto 0);
      we:      in std_logic;
      clk:     in std_logic;
      odata:   out std_logic_vector(sz-1 downto 0)
    );
  end component;

  signal s_sz:      natural := 4;
  signal s_addrw:   natural := 3;
  signal s_idata:   std_logic_vector(s_sz-1 downto 0);
  signal s_addr:    std_logic_vector(s_addrw-1 downto 0);
  signal s_we:      std_logic;
  signal s_clk:     std_logic;
  signal s_odata:   std_logic_vector(s_sz-1 downto 0);

begin
  uut: regfile port map (
    idata => s_idata,
    addr  => s_addr,
    we    => s_we,
    clk   => s_clk,
    odata => s_odata
  );

  process begin
    s_we <= '1';
    s_clk <= '0';
```

```

        wait for 250 ns;

        s_clk <= '1';
        s_addr <= "000";
        s_idata <= "0101";
        wait for 250 ns;

        s_clk <= '0';
        wait for 250 ns;

        s_clk <= '1';
        s_addr <= "001";
        s_idata <= "1101";
        wait for 250 ns;

        s_clk <= '0';
        wait for 250 ns;

        s_clk <= '1';
        s_addr <= "010";
        s_idata <= "0010";
        wait for 250 ns;

        s_clk <= '0';
        wait for 250 ns;

        s_clk <= '1';
        s_addr <= "011";
        s_idata <= "1001";
        wait for 250 ns;
    end process;
end behav;

```


1.5 regfile_ext.vhd

Το παρακάτω κύκλωμα υλοποιεί ένα register file με δύο επιπλέον θύρες.

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;
use ieee.numeric_std.all;

entity regfile_ext is
generic (
    sz:          natural := 4;
    addrw:       natural := 3
);
port (
    idata:       in std_logic_vector(sz-1 downto 0);
    raddr1:      in std_logic_vector(addrw-1 downto 0);
    raddr2:      in std_logic_vector(addrw-1 downto 0);
    waddr:       in std_logic_vector(addrw-1 downto 0);
    we:          in std_logic;
    clk:         in std_logic;
    rst:         in std_logic;
    odata1:      out std_logic_vector(sz-1 downto 0);
    odata2:      out std_logic_vector(sz-1 downto 0)
);
end regfile_ext;

architecture behav of regfile_ext is

    signal arrsz:          natural := 8;
    type regarr            is array(0 to arrsz-1) of std_logic_vector(sz-1 downto 0);
    -- Empty register array used for initialization when rst = 1.
    signal s_init:         regarr := (others => (others => '0'));
    signal regf:           regarr;

begin
    process (clk) begin
        if (rst = '1') then
            regf <= s_init;
        elsif (clk'event and clk = '0') then
            if (we = '1') then
                regf(to_integer(unsigned(waddr))) <= idata;
            end if;
        end if;
    end process;
    odata1 <= regf(to_integer(unsigned(raddr1)));
    odata2 <= regf(to_integer(unsigned(raddr2)));
end architecture;
```

```
        odata2 <= regf(to_integer(unsigned(raddr2)));  
end behav;
```

1.6 regfile_ext_tb.vhd

Testbench για το register file με δύο επιπλέον θύρες.

```
library ieee;
use ieee.std_logic_1164.all;

entity regfile_ext_tb is
end regfile_ext_tb;

architecture behav of regfile_ext_tb is

  component regfile_ext is
    generic (
      sz:          natural := 4;
      addrw:       natural := 2
    );
    port (
      idata:       in std_logic_vector(sz-1 downto 0);
      raddr1:      in std_logic_vector(addrw-1 downto 0);
      raddr2:      in std_logic_vector(addrw-1 downto 0);
      waddr:       in std_logic_vector(addrw-1 downto 0);
      we:          in std_logic;
      clk:         in std_logic;
      rst:         in std_logic;
      odata1:      out std_logic_vector(sz-1 downto 0);
      odata2:      out std_logic_vector(sz-1 downto 0)
    );
  end component;

  signal s_sz:          natural := 4;
  signal s_addrw:       natural := 2;
  signal s_idata:       std_logic_vector(s_sz-1 downto 0);
  signal s_raddr1:      std_logic_vector(s_addrw-1 downto 0);
  signal s_raddr2:      std_logic_vector(s_addrw-1 downto 0);
  signal s_waddr:       std_logic_vector(s_addrw-1 downto 0);
  signal s_we:          std_logic;
  signal s_clk:         std_logic;
  signal s_rst:         std_logic;
  signal s_odata1:      std_logic_vector(s_sz-1 downto 0);
  signal s_odata2:      std_logic_vector(s_sz-1 downto 0);

begin
  uut: regfile_ext port map (
    idata => s_idata,
    raddr1 => s_raddr1,
```

```

        raddr2 => s_raddr2,
        waddr => s_waddr,
        we => s_we,
        clk => s_clk,
        rst => s_rst,
        odata1 => s_odata1,
        odata2 => s_odata2
    );

```

```

process begin
    s_we <= '1';
    s_clk <= '0';
    s_rst <= '1';
    wait for 250 ns;

    s_clk <= '1';
    s_rst <= '0';
    s_waddr <= "00";
    s_idata <= "0101";
    wait for 250 ns;

    s_clk <= '0';
    wait for 250 ns;

    s_clk <= '1';
    s_waddr <= "01";
    s_idata <= "1101";
    wait for 250 ns;

    s_clk <= '0';
    wait for 250 ns;

    s_clk <= '1';
    s_rst <= '0';
    s_waddr <= "10";
    s_idata <= "0010";
    wait for 250 ns;

    s_clk <= '0';
    wait for 250 ns;

    s_clk <= '1';
    s_waddr <= "11";
    s_idata <= "1001";
    wait for 250 ns;

```

```

        s_clk <= '0';
        wait for 250 ns;

        s_we <= '0';
        s_clk <= '1';
        s_raddr1 <= "00";
        s_raddr2 <= "10";
        wait for 250 ns;


        s_clk <= '0';
        wait for 250 ns;

        s_we <= '0';
        s_clk <= '1';
        s_raddr1 <= "01";
        s_raddr2 <= "10";
        wait for 250 ns;
    end process;
end behav;


```

2 Εκτέλεση

2.1 reg_tb

 

2.2 regfile_tb

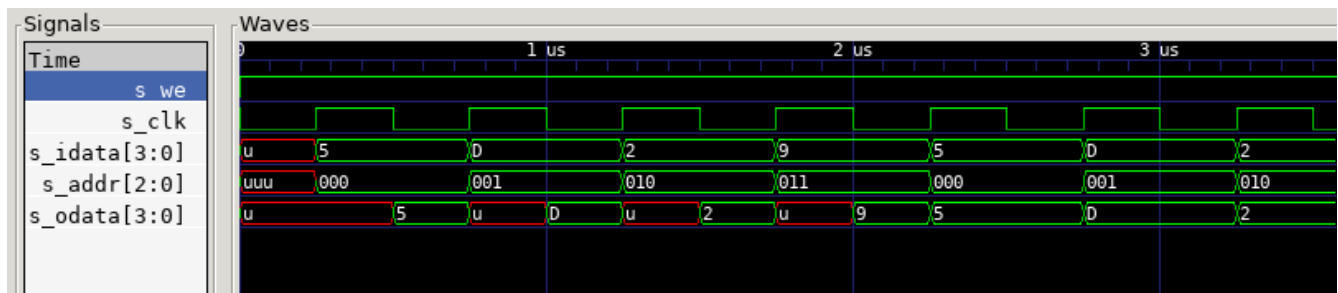

2.3 regfile_ext_tb

